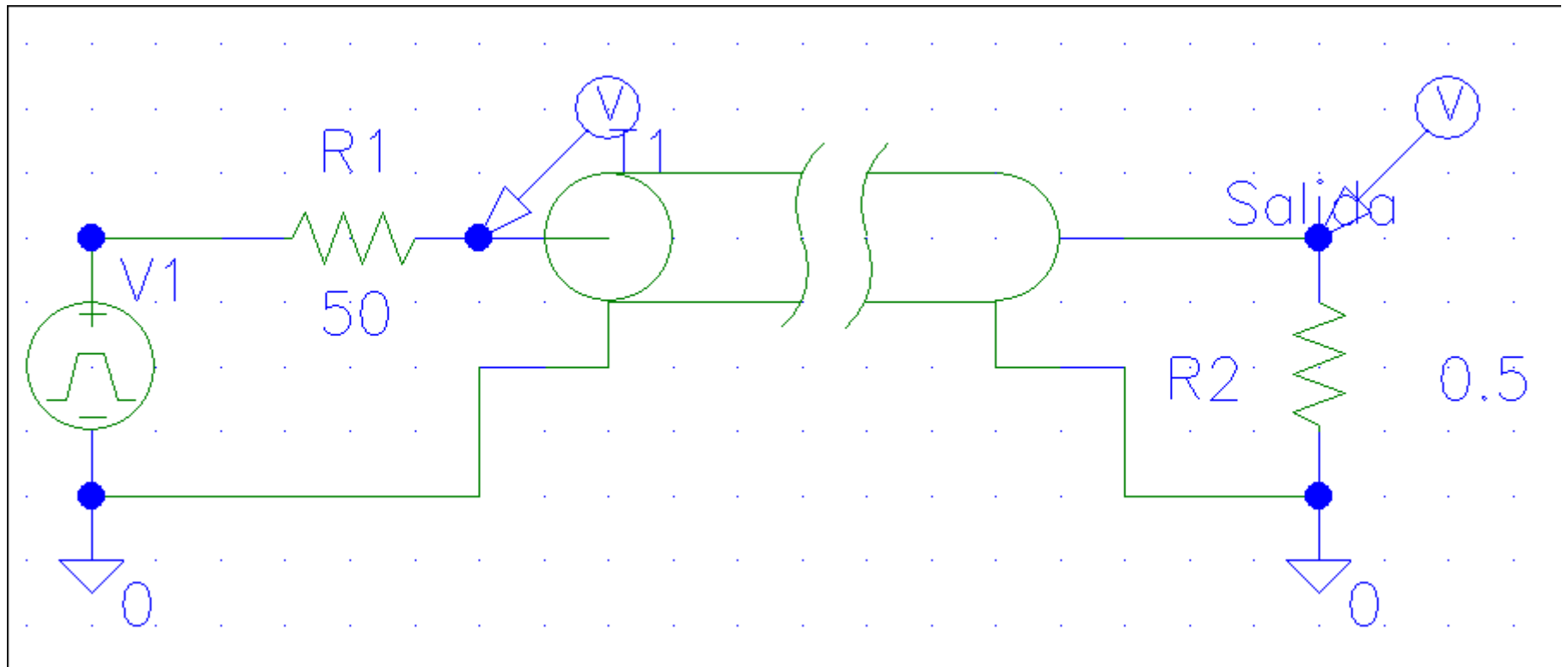



Práctica 4:

Simulación de líneas de transmisión

Circuito a simular con Pspice



Esquema eléctrico: cálculos

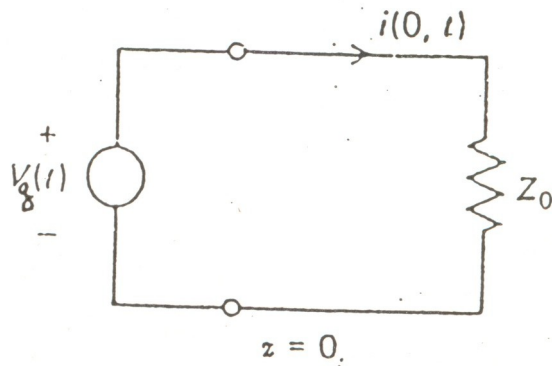

1 – Hallar Intensidad en $T=0, z=0$


$$i(z=0, t=0) = i_0 = V/R = V1/(R1+Z_0)$$

$$i_0 = V1/(R1+Z_0) = 5/(50+75) = 0.04 \text{ A}$$


2 – Hallar tensión en $T=0, z=0$

$$v(z=0, t=0) = V1 - i_0 * R1$$
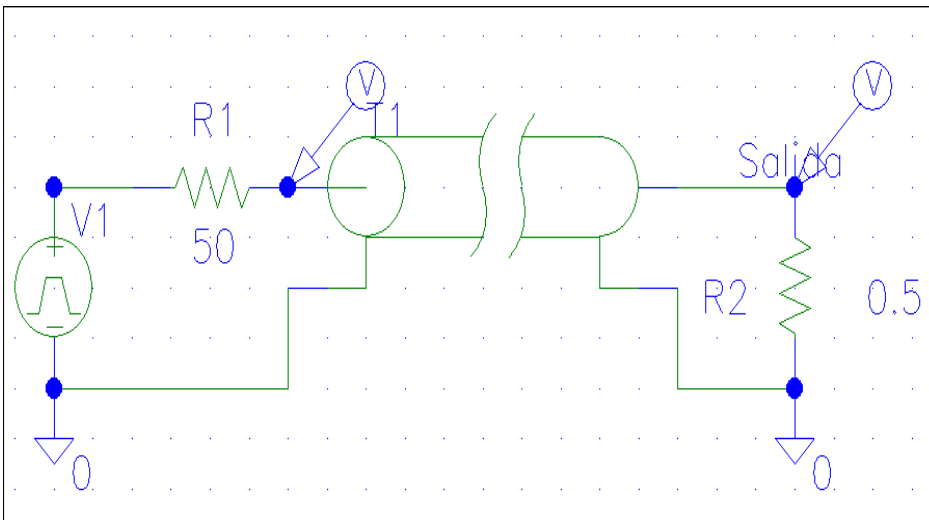
$$v(z=0, t=0) = 5 - 0.04*50 = 3 \text{ V}$$



Esquema eléctrico: cálculos

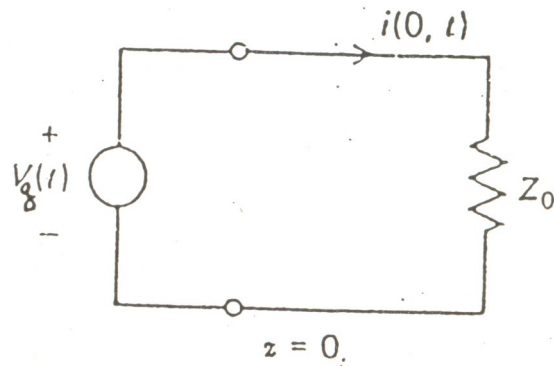

3 – Hallar V_- en T_p , $z=l$)

$$v(z=l, t=T_p) = V_+ + V_- = 3 - 3 = 0 \text{ V.}$$

$$C_{Ref. \text{ Carga}} = (R_2 - Z_0) / (R_2 + Z_0) = V_- / V_+$$

$$v(z=l, t=T_p) = 3 + V_- =$$

$$C_{Ref.} = (0.5 - 50) / (50 + 0.5) = -1 = V_- / V_+$$

$$V_- = -1 * V_+ = -3 \text{ V.}$$

4 – Hallar tensión en $2 T_p$, $3 T_p, \dots$

$$v(z=0, t=2T_p) = V_+ + V_- + V_{gen} =$$

$$C_{Ref. \text{ Gen.}} = (R_1 - Z_0) / (R_1 + Z_0) = V_- / V_+$$

$$V_{gen} = 0 \text{ V. (PER=1 ms., } 2T_p = 800 \text{ ns.)}$$

$$C_{Ref.} = (50 - 50) / (50 + 50) = 0 = V_- / V_+$$

$$V_- = 0 * V_+ = 0 \text{ V.}$$

$$V_+ = V_- \text{ de } v(z=l, t=T_p) = -3 \text{ V.}$$

$$v(z=0, t=2T_p) = -3 + 0 + 0 = -3 \text{ V.}$$

